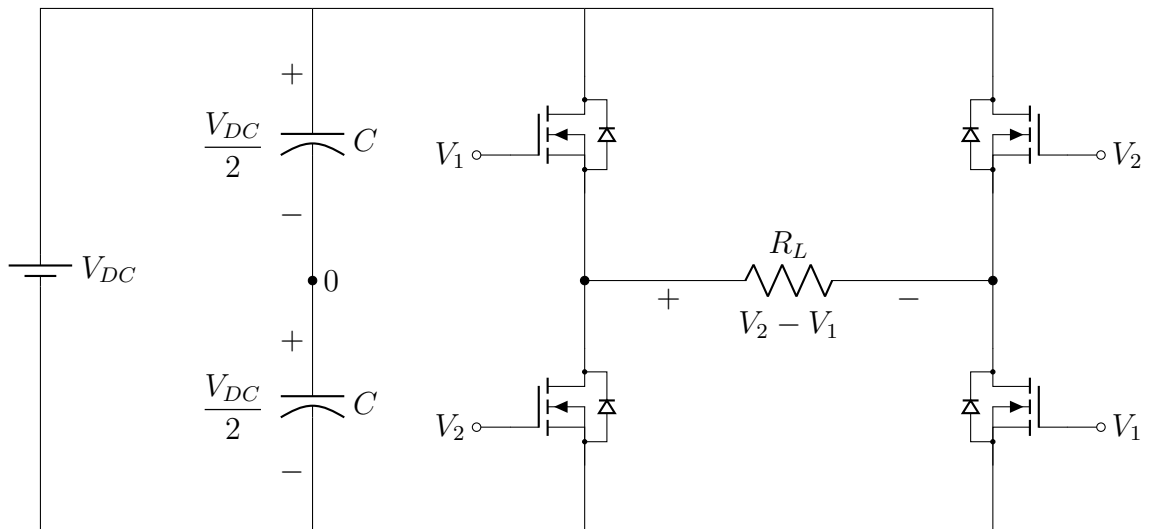


DC-AC Inverter (One phase)

Mario Eduardo Sepúlveda-Hernández

June 29, 2026



Where $V_{DC} = 12\text{V}$ and $C = 220\mu\text{F}$

The output voltage for the circuit is represented in the Figure 1

To activate the MOSFETS, you have to inject a pulse-train of $0 - 10\text{V}$ with a frequency of 60 Hz

The output voltage is going to be the voltage you measure in the load R_L

The output voltage is the orange signal from the Figure 1 and it's a voltage from -12V to $+12\text{V}$, i.e. a simulation of a single-phase generator

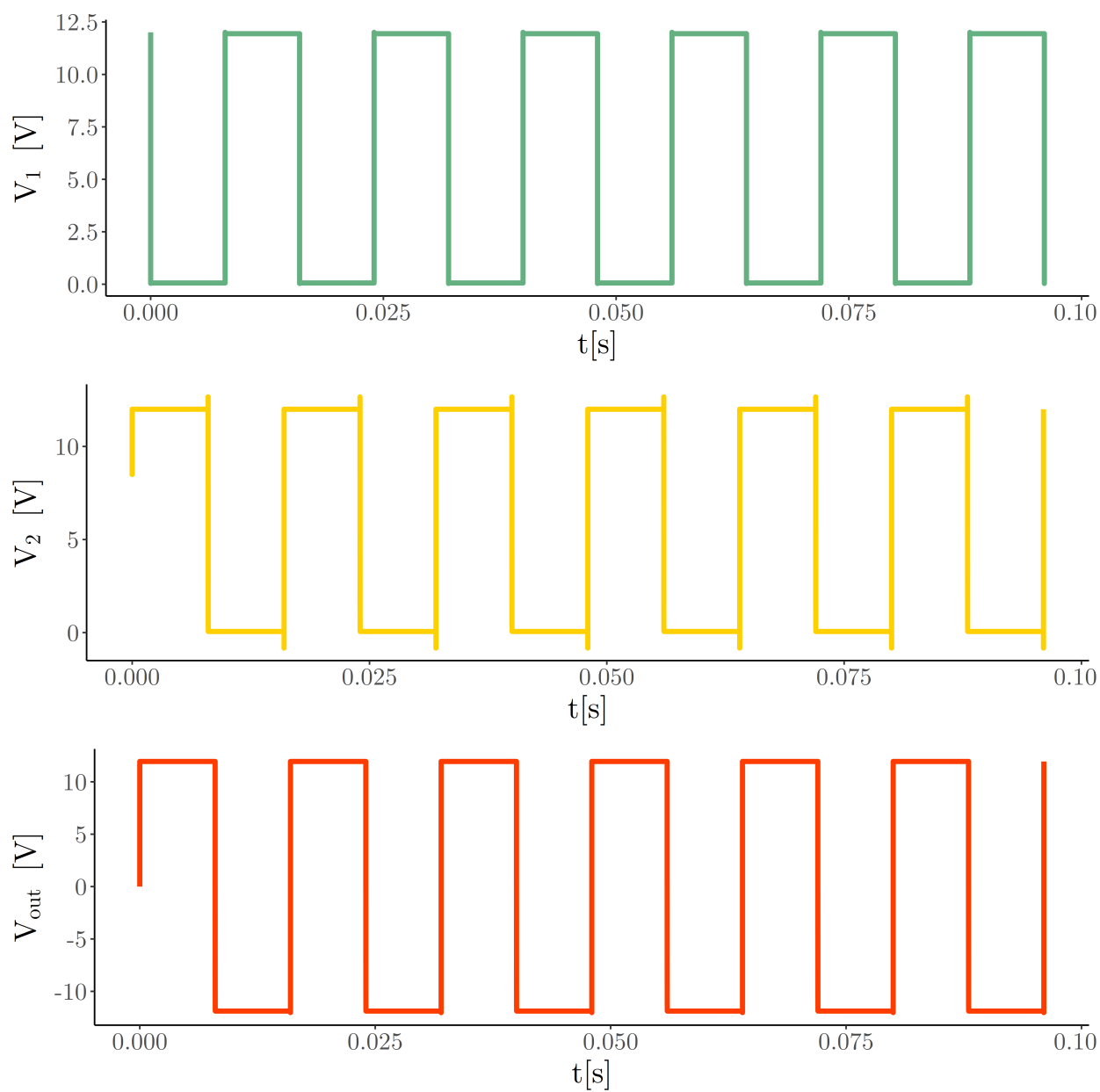


Figure 1: Output voltage from the inverter